



COLLEGE OF BUSINESS, PEACE, LEADERSHIP AND GOVERNANCE

NCSE115: FUNDAMENTALS OF DIGITAL ELECTRONICS

END OF SECOND SEMESTER EXAMINATIONS

MAY 2021

DR KANDIERO.A

TIME: 7 HOURS


INSTRUCTIONS

1. Answer any **ONE** question.
 2. Compile your answer into one consolidated PDF format document.
-


(b) Using the Logic simulator software

Draw and simulate the output of the following gates [30 marks]


(i)

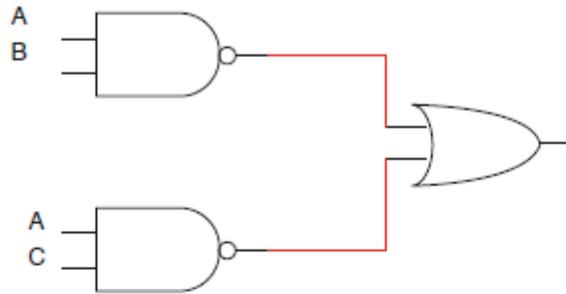

(i)

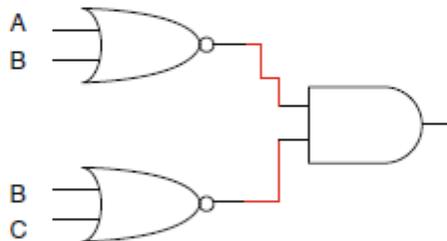

(ii)

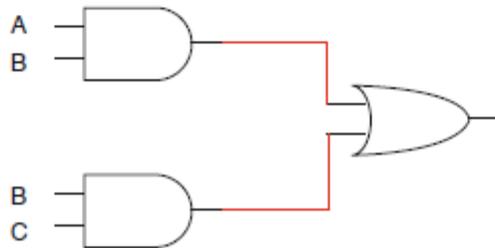

(iii) Simulate the truth tables of the logic diagrams above [10 marks]


(c) Using the logic simulator Draw logic circuits for the following function. [20 marks]

$$\overline{XYZ} + XZ + YZ$$

Question 2 [100]

Snip or make a screen shots of all your simulated drawing on a PDF answer document

Study the logic diagram below

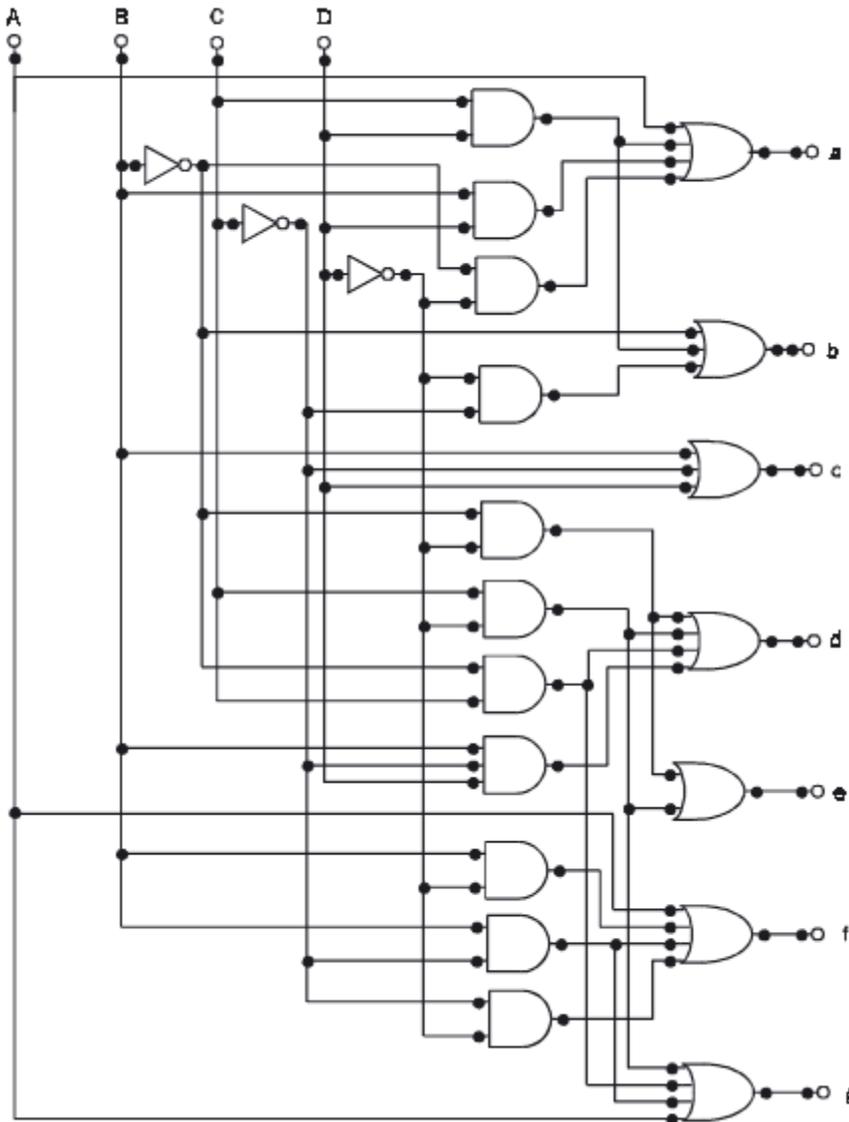

- (a) Deduce the Boolean expression for outputs a,b,c,d,e,f and g. [30 marks]
- (b) Simulate the above logic diagram using simulator software. [40marks]
- (c) Simulate the truth table. [30 marks]

Question 3 [100]

Snip or make a screen shot of all your simulated drawing to a PDF answer document

Study the Boolean expression shown below.

$$f = \bar{w}x\bar{y}z + \bar{w}xy\bar{z} + \bar{w}xyz + wx\bar{y}z$$

- (a) Using the logic simulator draw the logic diagram for the above Boolean expression **[30 marks]**
- (b) Using the K-map method simplify the Boolean expression above. **[30 marks]**
- (c) Hence using the logic simulator software draw the simplified logic diagram. **[40marks]**

END OF EXAMINATION
