



**COLLEGE OF BUSINESS, PEACE, LEADERSHIP AND GOVERNANCE**

**NCSC 116: FUNDAMENTALS OF DIGITAL ELECTROINCS**

**END OF FIRST SEMESTER EXAMINATIONS**

**NOVEMBER 2021**

**LECTURER: MR T MAKAMBWA.**

**TIME: 5 HOURS**

---

---

### ***INSTRUCTIONS***

Answer one question.

---

Credit will be awarded for logical, systematic and neat presentations

---

Use logsim simulator for the logic drawings


---

### QUESTION 1. [100]


For each the logic circuit given below draw the following logic diagrams

- determine the Boolean expression for the output  $X$ , construct the Corresponding truth table and simulate the Boolean expression. [60 marks]


(a)

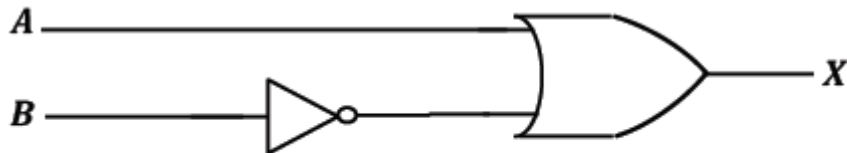

(b)

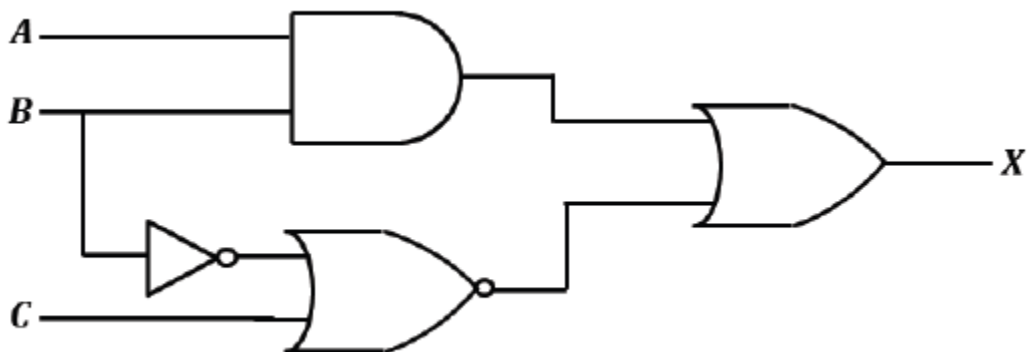

(c)

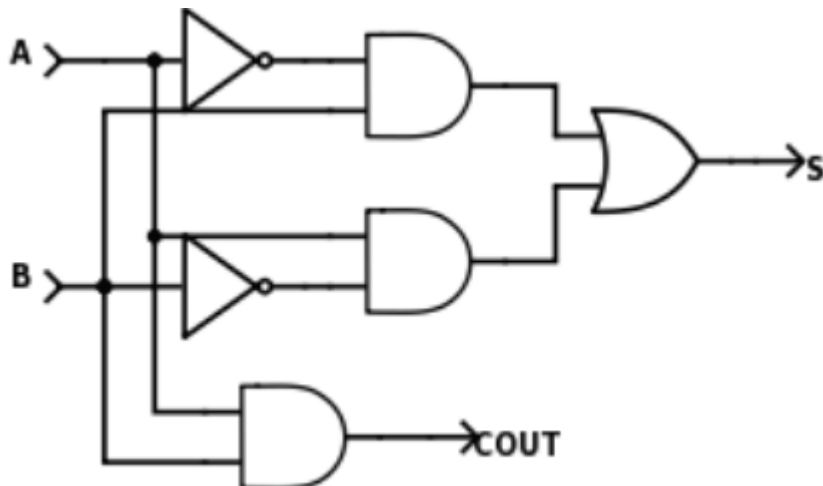

(d) Using the expression below draw the logic diagram and simulate the truth table. [40 marks]

$$Y = A.\overline{B}.\overline{C} + \overline{A}.B.\overline{C} + A.B.C + \overline{A}.\overline{B}.C$$

**Question 2. [100]**

(a) Using a logic gate simulator draw the logic circuit diagrams for the following gates

(i) NOT [2 marks]

(ii) AND [5 marks]

(iii) NAND [5 marks]

(iv) OR [5 marks]

(v) NOR [5 marks]


(vi) XOR [5 marks]

(vii) XNOR [5 marks]

(b) Reproduce the truth tables for the above logic gates [14 marks]

(c) Simulate the Boolean expression for each logic gate above. [14 marks]

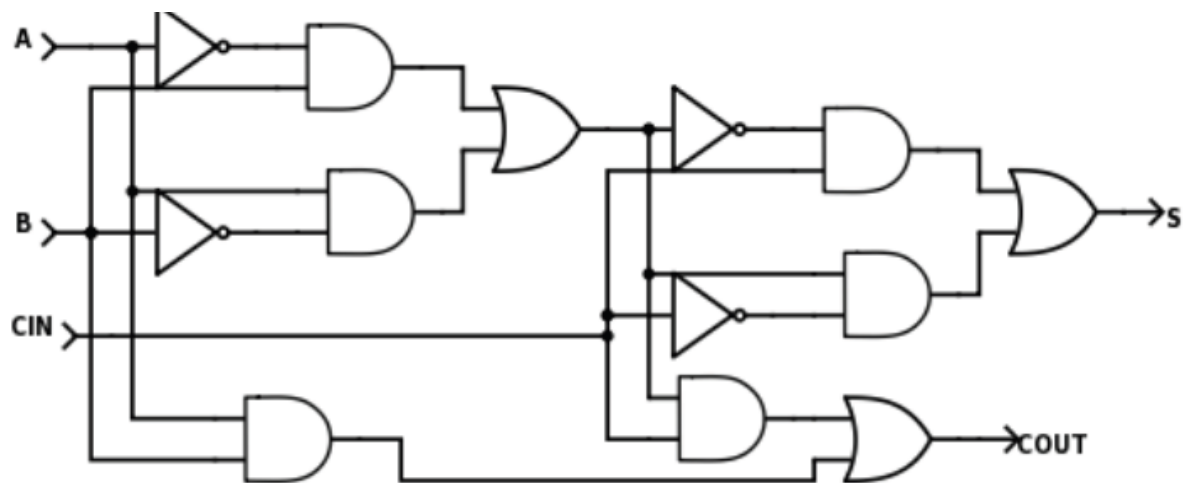(d) (i) Using a logic gate simulator draw the logic circuit diagram below. [30 marks]




(ii) Simulate the truth table. [5 marks]

(iii) Simulate the Boolean expression [5 marks]

### QUESTION 3


Draw the following logic diagrams:

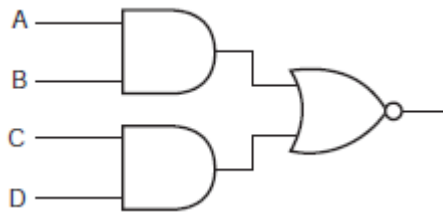- (i) Draw the logic diagrams
  - (ii) Simulate their truth tables
  - (iii) Boolean expression
- (a)




[15 marks]

(b)

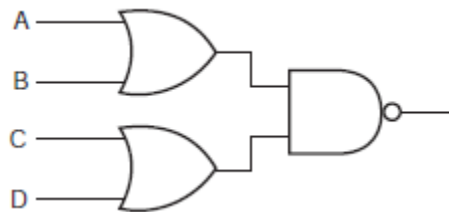


[15 marks]

(c)

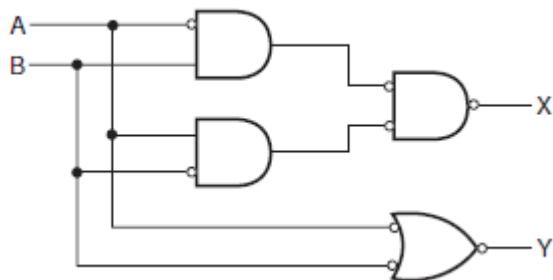

[15marks]

(d)

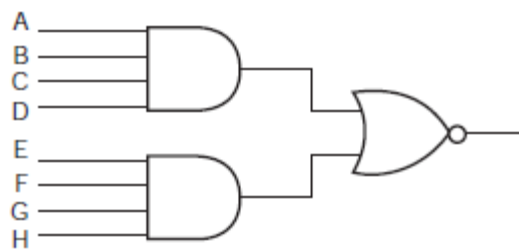

[15 marks]

(e) Draw the logic circuit diagram from the Boolean expression below. **[40 marks]**

(i)  $O = X + YZ$

(ii)  $x = \overline{A} B \overline{(A + BC)}$

(iii)  $x = A B \overline{C}$

(iv)  $z = (\overline{A} + B)(A + \overline{B})$

---

END OF PAPER